

- 1) 滿分 100 分，考試時間 2 小時。
- 2) 答案應有正確之數值與單位。
- 3) 可使用計算器，但不得使用電腦、行動電話等通訊器材。不得參閱任何書本及筆記。
- 4) 請確實遵守考試規則，違反考試規則者，依本校校規處置。

1. The switch in the circuit shown in **Fig. 1** moves from position 1 to position 2 at $t=0$. Find $v_o(t)$ for $t > 0$. (20%)
2. In the critically damped circuit of **Fig. 2**, the initial conditions are $i_L(0) = 2$ A and $v_C(0) = 5$ V. Find the voltage $v(t)$, for $t > 0$. (20%)

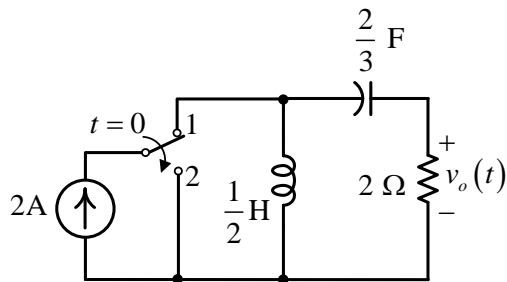


Fig. 1

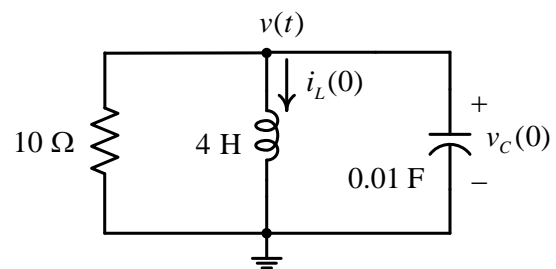


Fig. 2

3. The circuit of **Fig. 3** has been in steady-state before the switch moves from position 1 to position 2 at $t=0$. Find the voltage $v(t)$ for $t > 0$. (20%)
4. The switch in the circuit of **Fig. 4** closes at $t = 0$. If all the initial conditions are zero, find $v_C(t)$ for $t > 0$. (20%)

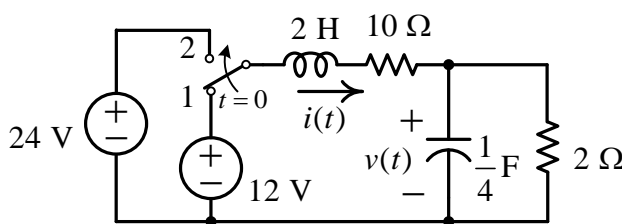


Fig. 3

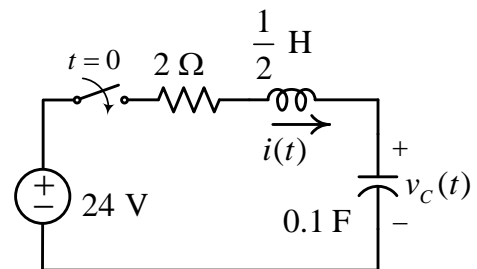


Fig. 4

5. Three branch currents in a network are known to be

$$i_1(t) = 2 \sin(377t + 45^\circ) \text{ A},$$


$$i_2(t) = 0.5 \cos(377t + 10^\circ) \text{ A},$$

$$i_3(t) = -0.25 \sin(377t + 60^\circ) \text{ A}.$$
 Determine the phase angles by which $i_1(t)$ leads $i_2(t)$, and $i_1(t)$ leads $i_3(t)$. (20%)

1. After the switch moves from position 1 to 2, the problem becomes solving a series R - L - C circuit without source, given the initial conditions $i_L(0)=2$ A and $v_C(0)=0$. The KVL equation can be written as

$$\frac{1}{2} \frac{di_L}{dt} + 2i_L + v_C = 0, \text{ with}$$

$$i_L = \frac{2}{3} \frac{dv_C}{dt}.$$

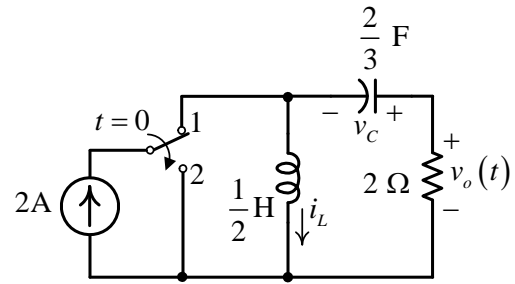

Combining the above two equations yields a 2nd-order ODE*

$$\frac{1}{3} \frac{d^2v_C}{dt^2} + \frac{4}{3} \frac{dv_C}{dt} + v_C = 0, \text{ which allows the characteristic equation to be obtained as}$$


$$s^2 + 4s + 3 = (s+1)(s+3) = 0. \text{ The natural frequencies are then } s=-1 \text{ and } s=-3 \text{ s}^{-1}.$$

The current i_L can be assumed to be $i_L = Ae^{-t} + Be^{-3t}$. With the initial condition, we obtain the 1st equation $i_L(0)=2=A+B$. The 2nd equation is given by

$$\left. \frac{di_L}{dt} \right|_{t=0} = -A - 3B = -4i_L(0) - 2v_C(0) = -8. \text{ Solving the two equations of } A \text{ and } B \text{ gives } A=-1 \text{ and}$$

$$B=3. \Rightarrow i_L = -e^{-t} + 3e^{-3t} \text{ A} \Rightarrow v_o = -2i_L = 2e^{-t} - 6e^{-3t} \text{ V, } t > 0.$$

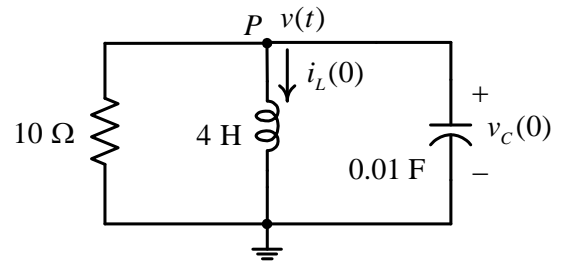2. Writing the KCL equation at node P yields
- $$\frac{v}{10} + i_L + 0.01 \frac{dv}{dt} = 0.$$
- Substituting $v = 4 \frac{di_L}{dt}$ to the KCL equation gives a 2nd-order ODE



$$\frac{d^2i_L}{dt^2} + 10 \frac{di_L}{dt} + 25 = 0, \text{ which gives the characteristic}$$

equation $s^2 + 10s + 25 = (s+5)^2 = 0$. A repeated root of $s=-5 \text{ s}^{-1}$ is found. The circuit is hence critically damped, and $v(t)$ must have the form $v = Ae^{-5t} + Bte^{-5t}$.


$$v(0) = A = 5, \quad 0.01 \left. \frac{dv}{dt} \right|_{t=0} = 0.01(-5A + B) = -\left(i_L(0) + \frac{v(0)}{10} \right) = -2.5 \Rightarrow B = -225$$

$$v = 5e^{-5t} - 225te^{-5t} \text{ V, } t > 0.$$

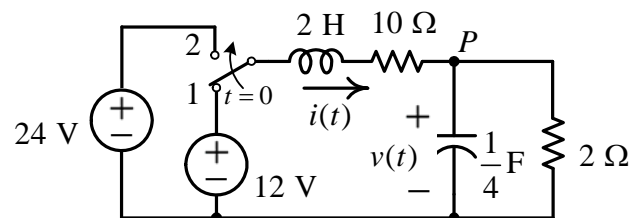3. Initial conditions $i(0) = \frac{12}{10+2} = 1$ A ,

$$v(0) = 12 \times \frac{2}{10+2} = 2 \text{ V. After the switch}$$

moves from position 1 to 2, the KVL equation is given by $-24 + 2 \frac{di}{dt} + 10i + v = 0,$



and the KCL equation at node P is $i = \frac{1}{4} \frac{dv}{dt} + \frac{v}{2}$. Substitution of i in KCL for i in KVL gives a 2nd-order ODE of v

* ODE: ordinary differential equation 常微分方程式

$\frac{d^2v}{dt^2} + 7\frac{dv}{dt} + 12v = 48$ with the characteristic equation $s^2 + 7s + 12 = (s + 3)(s + 4) = 0$. The voltage $v(t)$ must have the form $v = Ae^{-3t} + Be^{-4t} + k_p$.

The final value $v(\infty) = 24 \times \frac{2}{10 + 2} = 4 \text{ V} = k_p$.

The initial value $v(0) = 2 = A + B + 4 \Rightarrow A + B = -2$

The initial value $i(0) = 1 = \frac{1}{4} \frac{dv}{dt} \Big|_{t=0} + \frac{v(0)}{2} = \frac{1}{4}(-3A - 4B) + \frac{2}{2} \Rightarrow 3A + 4B = 0$

Solving for A and B yields $A = -8, B = 6$. $v = -8e^{-3t} + 6e^{-4t} + 4 \text{ V}, t > 0$

4. The KVL equation is given by $-24 + 2i + \frac{1}{2} \frac{di}{dt} + v_C = 0$.

The current i can be expressed as $i = 0.1 \frac{dv_C}{dt}$, which allows the KVL equation to be written as a 2nd-order ODE

$$\frac{d^2v_C}{dt^2} + 4\frac{dv_C}{dt} + 20v_C = 480.$$


The characteristic equation is $s^2 + 4s + 20 = 0 \Rightarrow s = -2 \pm j4 \text{ s}^{-1}$. The capacitor voltage v_C must have the form $v_C = e^{-2t}(A \cos 4t + B \sin 4t) + k_p$.

The final value $v_C(\infty) = 24 = k_p$.

The initial value $v_C(0) = 0 = A + 24 \Rightarrow A = -24$.

The initial value $i(0) = 0 = 0.1 \frac{dv_C}{dt} \Big|_{t=0} \Rightarrow -2A + 4B = 0 \Rightarrow B = -12$

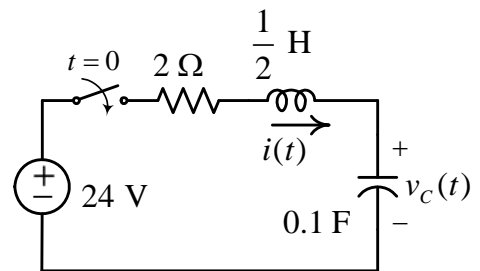$v_C = -e^{-2t}(24 \cos 4t + 12 \sin 4t) + 24 \text{ V}, t > 0$



5. Transform all the currents in cosine functions.

$$i_1(t) = 2 \sin(377t + 45^\circ) = 2 \cos(377t + 45^\circ - 90^\circ) = 2 \cos(377t - 45^\circ) \text{ A}$$

$$i_2(t) = 0.5 \cos(377t + 10^\circ) \text{ A}$$

$$i_3(t) = -0.25 \sin(377t + 60^\circ) = -0.25 \cos(377t + 60^\circ - 90^\circ) \\ = 0.25 \cos(377t + 60^\circ - 90^\circ + 180^\circ) = 0.25 \cos(377t + 150^\circ) \text{ A}$$

$i_1(t)$ leads $i_2(t)$ by $-45^\circ - 10^\circ = -55^\circ$,

$i_1(t)$ leads $i_3(t)$ by $-45^\circ - 150^\circ = -195^\circ$ or by $-195^\circ + 360^\circ = 165^\circ$